

Date: 25/04/18

Student Names: Metin Dumandağ, Fatih İver

Student IDs: 2015400048, 2016400264

Group ID: 16

Session ID: 1

## CMPE 240 Experiment 5 Preliminary Works

1. State Register Inputs: S1, S0
2. State Register Outputs: N1, N0
3. Combinational Block Inputs: A, B
4. Combinational Block Outputs: Y1, Y0
5. Is this a Moore or Mealy Machine? (No explanation, only short answer): Mealy
6. Draw the finite state machine.

