Student Names: Metin Dumandağ, Fatih İver

Section: 1 Group ID: 16

## **CMPE 240 Experiment 3 Preliminary Work**

## **Truth Table:**

#	Y1	Y0	<b>X2</b>	<b>X1</b>	<b>X0</b>	Z
0	0	0	0	0	0	0
1	0	0	0	0	1	0
2	0	0	0	1	0	1
3	0	0	0	1	1	1
4	0	0	1	0	0	0
5	0	0	1	0	1	1
6	0	0	1	1	0	0
7	0	0	1	1	1	1
8	0	1	0	0	0	0
9	0	1	0	0	1	1
10	0	1	0	1	0	0
11	0	1	0	1	1	1
12	0	1	1	0	0	0
13	0	1	1	0	1	1
14	0	1	1	1	0	0
15	0	1	1	1	1	1
16	1	0	0	0	0	1
17	1	0	0	0	1	1
18	1	0	0	1	0	1
19	1	0	0	1	1	1
20	1	0	1	0	0	0
21	1	0	1	0	1	1
22	1	0	1	1	0	0
23	1	0	1	1	1	0
24	1	1	0	0	0	1
25	1	1	0	0	1	1
26	1	1	0	1	0	0
27	1	1	0	1	1	0
28	1	1	1	0	0	1

Student Names: Metin Dumandağ, Fatih İver

Section: 1 Group ID: 16

29	1	1	1	0	1	0
30	1	1	1	1	0	0
31	1	1	1	1	1	0

## List of components used in the design:

- 1. 8-WAY MUX
- 2. 1 OR
- 3. 1 NAND
- 4.3 NOT

## **Circuit:**

